

1. Topological Sort

- a. The topological sort took a bit of time for me to wrap my head around. The recursive method mentioned in discussion didn't seem intuitive to me, so I tried to think of another method to use. The method I ended up using felt much simpler, I started by setting the Primary Inputs and Primary Outputs into their own vectors that I could iterate through later to print them, because I knew that as long as those two vectors went at the beginning and end, respectively, that the order within them didn't matter. I then put all of the Internal nodes into a map which I iteratively searched through, adding each node to an ordered vector of Internal nodes as I determined that all of the inputs for that node were either Primary Inputs or were Internal nodes that we had already seen. I used maps in addition to vectors to hold the PIs and POs so that I could use the find function to find them trivially, in addition to a map in parallel with my vector for Internal nodes that had already been seen, for the same reason. After all of that it was a simple matter of printing all of the names in order to standard output.
- b. All of this was done inside of circuit.cpp because that was where all of the necessary data was.

2. Functional Simulation

- a. Functional Simulation I quickly realized was fairly trivial once a topological sort was done. Therefore, I began the simulation by simply recreating the same data structures from my topological sort and sorting the nodes in the same way. From there, it simply followed that I had to apply the read-in values to the Primary Inputs, and cascade them down through the gates in topological order to reach the Primary Outputs at the end. I had initially presumed that the cascading part would be simple, but I quickly was reminded that I would have to penetrate the truthtable data structure in order to glean whether each gate was a NOT, OR, or AND. The method I came up with for doing this I thought was fairly clever, knowing that NOT gates only ever have 1 input, I checked the number of variables to determine if it could be a NOT gate. If there was only one, I also knew that under that circumstance OR and AND behave identically, so the only question was whether it was a NOT or as I termed it, a NOTNOT. I wasn't sure if this was going to be tested so I went ahead and assumed it would be. Outside of that, if there was more than 1 variable, I would check how many rows there were. If there was 1 row, then it was an AND gate, otherwise it was an OR, because there's only ever 1 instance where an AND gate is true. When I proceeded to parse these, NOTs flipped the incoming bit, and NOTNOTs simply propagated it. For ORs I set the outgoing bit initially to 0, and then flipped it to 1 if I found any of the inputs to be 1. Likewise, for ANDs I set it to 1, and if I found a 0 I set it to 0.